 


Recognizing and Reducing Data Acquisition Switching Transients

Application Note 1444



Introduction

If you make sequential measurements with a data acquisition/switch unit or data logger, you could be having problems and not even realize it. Transients in your switching system can wreak havoc with your measurement results, cause crosstalk between channels or damage your relays.

This application note is intended to help you recognize, understand and resolve problems associated with switching transients. We will use the Agilent 34970A data acquisition/switch unit in our examples, but the principles we discuss are applicable to data acquisition/switch units and switch cards from any test-equipment vendor.

Symptoms of transients in switching systems

How do you know if you are experiencing transient voltage or current in your switching system?

Here are some common symptoms:

- Digital logic connected to the switch card resets or is erratic
- Voltage from previous channel appears unexpectedly as an output on the next channel
- Your data acquisition/switch system resets or hangs
- Voltages across the relay/switch are twice the applied voltage
- The life of your relay/switch is unexpectedly low
- Sensitive devices in the DUT (device under test) are damaged



Agilent Technologies

What causes transients?

When you are using a 34970A data acquisition/switch unit with a switch card such as the 34901A, low impedance sources can produce large and fast current transients. These high-current transients may appear to be caused by simultaneous contact closure, but they are actually caused by measurement circuitry stray capacitances. The current transients may cause problems with adjacent channels, create transients in the ground circuit that upset digital logic connected to the device under test, or in some cases, cause the 34970A to reset or hang.

To understand these transients, we must consider the stray capacitance found in measurement circuitry. Figure 1 shows connections that can cause the above-described symptoms. Figure 1 shows the stray capacitances C1 (~120 pF) and C2 (~70 pF) associated with the inputs to the DMM to ground. Channel 1 is connected to measure a low-value resistor that is connected to ground. Channel 2 is connected to measure the current of a load connected to a 25 Vdc power supply. The sense resistor is 0.1 ohm. Channel 3 represents a resistor measurement.

 


Figure 1: C1, C2 represent stray capacitance that can create transient currents and voltages.

Example 1

Now we will take a look at what happens when we scan through channel 1, channel 2, and channel 3.

Channel 1 closes

When channel 1 closes, the voltages on capacitors C1, C2 are discharged and the voltages across both capacitors rapidly approach zero.

Channel 2 closes

When channel 2 closes after channel 1 opens, the 25 Vdc from the power supply quickly charges both capacitors. The series resistance of the circuit is the output resistance of the power supply (<0.1 ohm), the shunt resistor (for C2 only), the resistance of the traces on the PC board, the relay contact resistance (<0.1 ohm) and finally the ground path back to the power supply. This total resistance will be less than 1 ohm. The initial surge current will be more than 25 amps through each contact. These large, fast transient currents cause havoc with digital circuits. Power supply voltages greater than 100 volts may create transients that interfere with proper operation of the data acquisition system.

The large transient currents create arcing across the relay contacts as they close, which causes movement of metal from one relay contact to the other, or other deterioration of the contact surface, and reduces the life of the relay. These transients are of short duration and are difficult to measure.

After channel 2 relays open, C1, C2 are both charged to approximately +25 volts.

Channel 3 closes

When channel 3 closes, C1 will discharge a large current pulse through the ground circuit (creating large currents similar to those that occurred when channel 2 closed). Channel 3 Lo relay will likely wear out faster than channel 3 Hi. The 25 volts on C2 will initially be seen across the 10k ohm resistor. The voltage will be across the 10k ohm resistor as a transient until it is discharged. You will see it as an output from the high to low terminals of the channel, and you may even interpret it as a failure of channel 2. The symptom is similar to having channel 3 close before channel 2 opens. Actually, channel 2 does open before channel 3 closes.

Example 2

An unexpected voltage also manifests itself when the source is floating (very high impedance to ground, see figure 2). After channel 1 closes, C1 and C2 are in series and will charge such that 25 V is present between points A and B. When channel 1 opens the +25 V at point A referenced to B remains. When channel 2 closes, one of the contacts will close before the other. Assume the lower of the two contacts closes first. Now C will be -25 V referenced to B and the voltage across the upper channel 2 contact will be 50 V. In this case the sum of both voltage sources must be less than the rating of the relay.

A severe case occurs when you measure AC line voltage on two successive channels; the voltage across the relay of the second channel may be twice the peak voltage and create very large currents and arcing.

How to solve transient problems

To reduce the current transients that create problems in the digital circuits associated with the measurement and reduce the life of the relay contacts, place a resistor of 100 ohms in series with the Hi and/or Lo channel terminal that is connected to a low impedance source or to ground. The current limit resistor will not deteriorate voltage measurement but will limit the peak current. Placing the current sense resistor at the low side of the power supply will also avoid the high voltages.

You can prevent the voltage of one channel transferred to the subsequent channel by setting up an intermediate channel that has the Lo and Hi tied to ground through a 100 ohm resistor to discharge C1 and C2. This channel may be activated after switching voltages higher than can be tolerated by a subsequent measurement.

Conclusion

The switching transient problems discussed in this application note are common. Fortunately, they can be reduced using the techniques described in this application note, to eliminate problems.

Glossary

Transient — transition behavior until a steady state is achieved, may be initiated by a contact closure

Related Agilent Literature

Data sheet — 34970A Data Acquisition/Switch Unit, pub. no. 5965-5290EN

 


Figure 2: Floating sources can create current and voltage transients in adjacent channels.

www.agilent.com



Agilent Email Updates

www.agilent.com/find/emailupdates

Get the latest information on the products and applications you select.

Agilent T&M Software and Connectivity

Agilent's Test and Measurement software and connectivity products, solutions and developer network allows you to take time out of connecting your instruments to your computer with tools based on PC standards, so you can focus on your tasks, not on your connections.

Visit www.agilent.com/find/connectivity for more information.

By internet, phone, or fax, get assistance with all your test & measurement needs

Online assistance: www.agilent.com/find/assist

Phone or Fax

United States:

(tel) 800 452 4844

Canada:

(tel) 877 894 4414

(fax) 905 282 6495

China:

(tel) 800 810 0189

(fax) 800 820 2816

Europe:

(tel) (31 20) 547 2323

(fax) (31 20) 547 2390

Japan:

(tel) (81) 426 56 7832

(fax) (81) 426 56 7840

Korea:

(tel) (82 2) 2004 5004

(fax) (82 2) 2004 5115

Latin America:

(tel) (305) 269 7500

(fax) (305) 269 7599

Taiwan:

(tel) 0800 047 866

(fax) 0800 286 331

Other Asia Pacific Countries:

(tel) (65) 6375 8100

(fax) (65) 6836 0252

(e-mail) tm_asia@agilent.com

Product specifications and descriptions in this document
subject to change without notice.

© Agilent Technologies, Inc. 2003

Printed in the USA March 3, 2003

5988-8996EN



Agilent Technologies